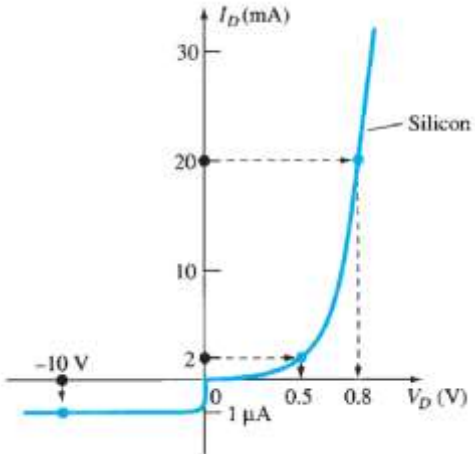
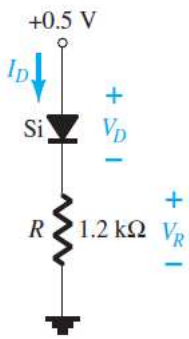


**1<sup>st</sup> SEMESTER EXAMINATION, 2022 – 23**  
**First Year, B. Tech. – Common to All Branch**  
**BASIC ELECTRONICS ENGINEERING**


Duration: 3:00 hrs

Max Marks: 100

*Note: - Attempt all questions. All Questions carry equal marks. In case of any ambiguity or missing data, the same may be assumed and state the assumption made in the answer.*

<p>Q 1.</p>	<p>Answer any four parts of the following.</p> <p>a) Describe the difference between <math>n</math> -type and <math>p</math> -type semiconductor materials. Define an intrinsic material, a negative temperature coefficient, and covalent bonding.</p> <p>b) Compare P-N junction diode and zener diode on the basis of:</p> <p>(i) Symbol (ii) Direction of conduction (iii) Reverse breakdown (iv) Application (v) Resistance in reverse biased condition</p> <p>c) What is an LED? Explain its working principle. Write the advantages, and application of LED.</p> <p>d) Draw VI characteristics of PN junction diode and explain it.</p> <p>e) Determine the dc resistance levels for the diode of Fig. 1 at</p> <p>(i) <math>I_D = 2</math> mA (low level)</p> <p>(ii) <math>I_D = 20</math> mA (high level)</p> <p>(iii) <math>V_D = -10</math> V (reverse-biased)</p> <div style="text-align: center;">  <p>Fig. 1</p> </div> <p>f) For the series diode configuration of Fig. 2, determine <math>V_D</math>, <math>V_R</math>, and <math>I_D</math>.</p> <div style="text-align: center;">  <p>Fig. 2</p> </div>	<p>5x4=20</p>
-------------	---	---------------

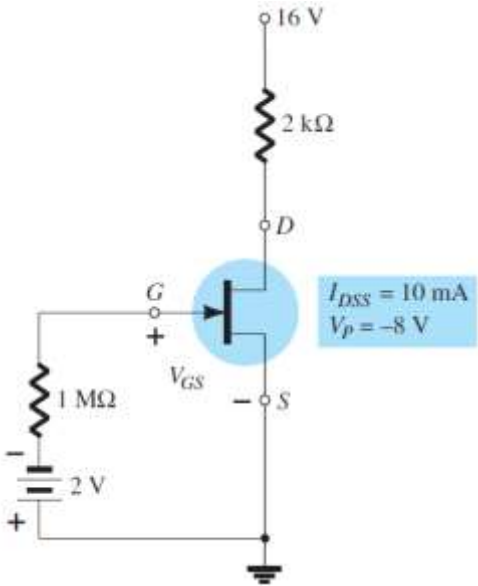

	<p>b) Define <math>\alpha</math> and <math>\beta</math> with respect to BJT and derive the relationship between them. A transistor having <math>\beta = 100</math> and reverse saturation current <math>I_{CEO} = 150 \mu A</math> is operated in CE mode. If the base current is 0.2 mA. Calculate <math>I_E</math>, <math>I_C</math> and <math>\alpha</math>.</p> <p>c) Compare CB, CE and CC configuration on the basis of: (i) Input impedance (ii) Output impedance (iii) Current gain (iv) Voltage gain (v) Phase angle (vi) Power gain (vii) Application</p>	
Q 4.	<p>Answer any two parts of the following.</p> <p>a) Sketch and explain the construction of n-channel JFET and also explain its working.</p> <p>b) Explain working principle of N-channel depletion type MOSFET with construction diagram. Also draw its transfer and drain characteristics.</p> <p>c) Determine the following for the network of Fig. 7</p> <p>(i) <math>V_{GSQ}</math>  (ii) <math>I_{DQ}</math>  (iii) <math>V_{DS}</math>  (iv) <math>V_D</math>  (v) <math>V_G</math>  (vi) <math>V_S</math></p>  <p style="text-align: center;">Fig. 7</p>	10x2= 20
Q 5.	<p>Answer any two parts of the following.</p> <p>a) Minimize using K-map and realize using NOR gates only. <math>F(A,B,C,D) = \prod(3,4,5,7,9,13,14,15).d(0,2,8)</math></p> <p>b) Draw and explain the working of inverting, non-inverting, and summing amplifier using OP-AMP.</p> <p>c) Perform following operation as indicated:</p> <p>(i) Convert <math>(25.125)_{10}</math> into Haxadecimal number.</p> <p>(ii) Determine the base of following: <math>(312)_B = (54)_{10}</math></p> <p>(iii) Write the truth table of two input X-OR gate and two input X-NOR gate.</p> <p>(iv) Simplified the boolean equation <math>X = [(A + \bar{B})(B + C)]B</math></p> <p>(v) Draw the circuit diagram to implement the following equation:  <math>X = [(A + B)(\bar{B} + C)]</math></p>	10x2= 20

\*\*\*\*\*