


II SEMESTER EXAMINATION, 2022 – 23
First Year , B.Tech – All Branches
Basic Electronics Engineering

Duration: 3:00 hrs

Max Marks: 100

Note: - Attempt all questions. All Questions carry equal marks. In case of any ambiguity or missing data, the same may be assumed and state the assumption made in the answer.


<p>Q 1.</p>	<p>Answer any four parts of the following.</p> <p>a) Describe (i) the formation of depletion region, (ii) Forward Biasing, (iii) Reverse Biasing.</p> <p>b) How Zener diode works as a voltage regulator? Explain with the help of its characteristics.</p> <p>c) What do you understand by doping? Explain intrinsic and extrinsic semiconductor with appropriate examples and figures.</p> <p>d) Calculate the current through $48\ \Omega$ resistor in the circuit shown in Fig. 3. Assume the diodes to be of silicon and forward resistance of each diode is $1\ \Omega$.</p> <div data-bbox="483 926 935 1213" data-label="Diagram"> </div> <p>e) What are the two main types of diode breakdown mechanisms? Describe each mechanism and how they occur.</p> <p>f) For the circuit shown in Figure, find the maximum and minimum values of zener diode current.</p> <div data-bbox="448 1402 987 1671" data-label="Diagram"> </div>	<p>5x4=20</p>
<p>Q 2.</p>	<p>Answer any four parts of the following.</p> <p>a) With respect to half wave rectifier explain (i) ripple factor, (ii) Power efficiency.</p> <p>b) An a.c. supply of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 10 : 1. Find (i) the output d.c. voltage and (ii) the peak inverse voltage. Assume the diode to be ideal.</p> <p>c) Explain Biased series clipper with input and output waveforms.</p> <p>d) A full-wave rectifier uses two diodes, the internal resistance of each diode may be assumed constant at $20\ \Omega$. The transformer r.m.s. secondary voltage from centre tap to each end of secondary is 50 V and load resistance is $980\ \Omega$. Find: (i) the mean load current (ii) the r.m.s. value of load current.</p>	<p>5x4=20</p>

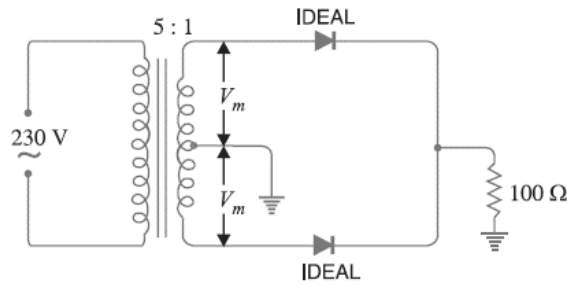

- d) Compare half wave rectifier with full wave rectifier on the basis of their parameters.
- e) How does a positive clamper circuit work? Explain its operation and waveform transformation.
- f) How does a bridge rectifier circuit convert an alternating current (AC) input into a direct current (DC) output? Write the advantages of using a bridge rectifier over a center-tapped full-wave rectifier?

Q 3. **Answer any two parts of the following.**

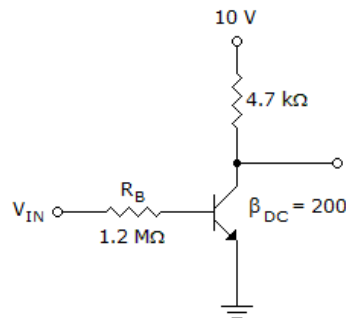
- a) Draw CE configuration of transistor. Sketch and explain input and output characteristics for NPN transistor.
- b) Refer to the below figure. Determine the minimum value of I_B that will produce saturation.



- c) Explain the concept of biasing in BJT circuits. What are the different methods of biasing? Explain any one method in detail.

Q 4. **Answer any two parts of the following.**

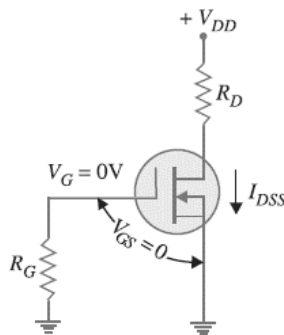
- a) What is FET? Classify it and differentiate between FET and BJT.
- b) Determine the drain-to-source voltage (V_{DS}) in the circuit shown in Fig. If $V_{DD} = +18V$ and $R_D = 620\Omega$. The MOSFET data sheet gives $V_{GS}(\text{off}) = -8V$ and $I_{DSS} = 12\text{ mA}$.



- c) Explain the construction and working of Enhancement mode MOSFET with neat diagram.

Q 5. **Answer any two parts of the following.**

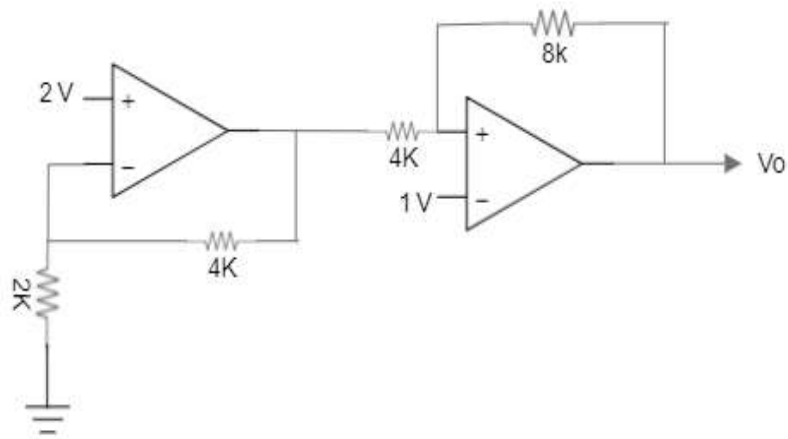- a) Explain operational amplifier can be used as a differentiator and integrator.
- b) Calculate output voltage in circuit shown in figure below.



c) Define the following with respect to the operational amplifier.

- (i) CMRR
- (ii) Slew rate
- (iii) Input offset voltage
- (iv) output offset voltage
- (v) Concept of Virtual Ground.
