

III SEMESTER EXAMINATION, 2022 – 23
IInd yr B.Tech. – E&CE/EE/E&EE
Networks Analysis and Synthesis


Duration: 3:00 hrs

Max Marks: 100

Note: - Attempt all questions. All Questions carry equal marks. In case of any ambiguity or missing data, the same may be assumed and state the assumption made in the answer.

<p>Q 1.</p>	<p>Answer any four parts of the following.</p> <p>a) State and explain Millman's theorem</p> <p>b) What is meant by symmetry in a two-port network? Determine the condition of symmetry in terms of hybrid parameters for a two-port network.</p> <p>c) Define positive real function and mention its properties</p> <p>d) Find the Laplace transform of the periodic waveform</p> <div data-bbox="292 840 779 1092"> </div> <p>e) For the graph shown in fig select 1,2,3 as twigs of a tree, write the f-loop and f- cutset matrices</p> <div data-bbox="178 1218 519 1533"> </div> <p>f) Describe the singularity function with suitable examples.</p>	<p>5x4=20</p>
<p>Q 2.</p>	<p>Answer any four parts of the following.</p> <p>a) Draw the directed graph of the incidence matrix given below. Mathematically find out fundamental cutset matrix</p> $A = \begin{bmatrix} 1 & 0 & 0 & -1 & 0 & 1 \\ -1 & 0 & 1 & 0 & 1 & 0 \\ 0 & 1 & -1 & 0 & 0 & 0 \end{bmatrix}$	<p>5x4=20</p>

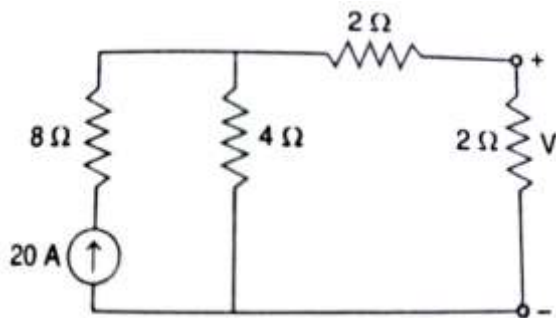b) For the circuit shown, verify the reciprocity theorem



c) For the network to be reciprocal show that $AD - BC = 1$, where A, B, C, D are the Transmission line parameters.

d) Find the Laplace transform for the given signal and calculate the ROC.

$$x(t) = t^2 e^{-3t} u(t)$$

e) Write the properties of RL driving point impedance function


f) Find the step response of series RL circuit

Q 3.


Answer any two parts of the following.

10x2= 20

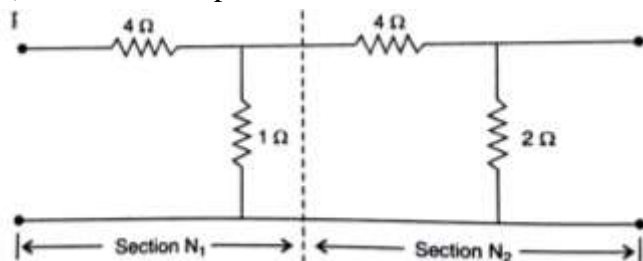a) Determine T-parameters for cascade connected network shown below



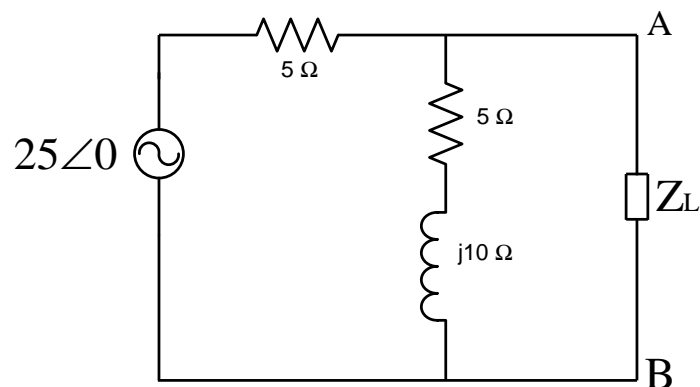b) Calculate the value of Z_L to be connected across A-B for maximum power transfer and also find power absorbed by Z_L for the circuit given below



c) Determine the term 'tree' 'f-cutset' and f-loops' related to linear graph and discuss their properties


Q 4.

Answer any two parts of the following.

10x2= 20

a) Explain the following terms:

- (i) Tree and co-tree
- (ii) Node and branch
- (iii) Twig and Link or chord
- (iv) Oriented or directed graph
- (v) Connected and un-connected graph

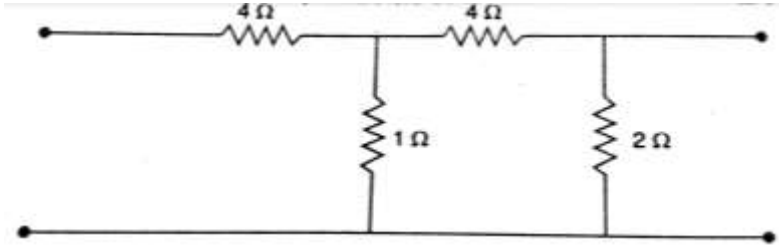	<p>b) State and explain Thevenin's theorem and specify the types of circuits to which it is applicable. Also state the theorem which is dual of the above theorem.</p> <p>c) Realize $Y(s) = \frac{(s+1)(s+6)}{(s+2)}$ in Foster- II form.</p>	
Q 5.	<p>Answer any two parts of the following.</p> <p>a) Realize $Z(s) = \frac{s^4 + 7s^2 + 9}{s^3 + 4s}$ in Causer-I and II forms</p> <p>b) Determine Z and Y- parameters of the network shown below</p>  <p>c) Find the step response of series RLC circuit.</p>	10x2= 20
