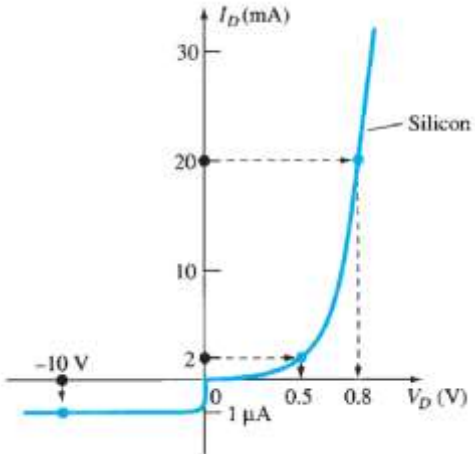
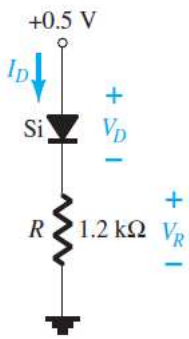



1st /2nd SEMESTER EXAMINATION, 2022 – 23
First Year, B. Tech. – Common to All Branch
FUNDAMENTAL OF ELECTRONICS ENGINEERING

Duration: 3:00 hrs

Max Marks: 100

Note: - Attempt all questions. All Questions carry equal marks. In case of any ambiguity or missing data, the same may be assumed and state the assumption made in the answer.

Q 1.	<p>Answer any four parts of the following.</p> <p>a) Describe the difference between n -type and p -type semiconductor materials. Define an intrinsic material, a negative temperature coefficient, and covalent bonding.</p> <p>b) Compare P-N junction diode and zener diode on the basis of: (i) Symbol (ii) Direction of conduction (iii) Reverse breakdown (iv) Application (v) Resistance in reverse biased condition</p> <p>c) What is an LED? Explain its working principle. Write the advantages, and application of LED.</p> <p>d) Draw VI characteristics of PN junction diode and explain it.</p> <p>e) Determine the dc resistance levels for the diode of Fig. 1 at (i) $I_D = 2$ mA (low level) (ii) $I_D = 20$ mA (high level) (iii) $V_D = -10$ V (reverse-biased)</p> <div style="text-align: center;">  <p>Fig. 1</p> </div> <p>f) For the series diode configuration of Fig. 2, determine V_D, V_R, and I_D.</p> <div style="text-align: center;">  <p>Fig. 2</p> </div>	5x4=20
------	---	--------

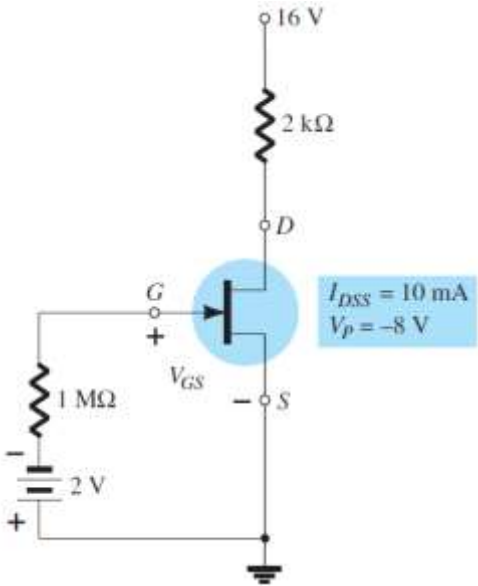	<p>b) Define α and β with respect to BJT and derive the relationship between them. A transistor having $\beta = 100$ and reverse saturation current $I_{CEO} = 150 \mu A$ is operated in CE mode. If the base current is 0.2 mA. Calculate I_E, I_C and α.</p> <p>c) Compare CB, CE and CC configuration on the basis of: (i) Input impedance (ii) Output impedance (iii) Current gain (iv) Voltage gain (v) Phase angle (vi) Power gain (vii) Application</p>	
Q 4.	<p>Answer any two parts of the following.</p> <p>a) Sketch and explain the construction of n-channel JFET and also explain its working.</p> <p>b) Explain working principle of N-channel depletion type MOSFET with construction diagram. Also draw its transfer and drain characteristics.</p> <p>c) Determine the following for the network of Fig. 7</p> <p>(i) V_{GSQ} (ii) I_{DQ} (iii) V_{DS} (iv) V_D (v) V_G (vi) V_S</p>  <p style="text-align: center;">Fig. 7</p>	10x2= 20
Q 5.	<p>Answer any two parts of the following.</p> <p>a) Minimize using K-map and realize using NOR gates only. $F(A,B,C,D) = \prod(3,4,5,7,9,13,14,15).d(0,2,8)$</p> <p>b) Draw and explain the working of inverting, non-inverting, and summing amplifier using OP-AMP.</p> <p>c) Perform following operation as indicated:</p> <p>(i) Convert $(25.125)_{10}$ into Haxadecimal number.</p> <p>(ii) Determine the base of following: $(312)_B = (54)_{10}$</p> <p>(iii) Write the truth table of two input X-OR gate and two input X-NOR gate.</p> <p>(iv) Simplified the boolean equation $X = [(A + \bar{B})(B + C)]B$</p> <p>(v) Draw the circuit diagram to implement the following equation: $X = [(A + B)(\bar{B} + C)]$</p>	10x2= 20
